

The Wheatstone Bridge

P. Reany

February 12, 2023

Abstract

This paper presents the Wheatstone Bridge in its ‘simplest’ form.

The purpose of the Wheatstone Bridge is to measure the resistance of an unknown resistance, which I have labeled as R_x in Fig. 1. We need a formula, and to get that formula, all we will use is Ohm’s Law. Other derivations use Kirchoff’s Law.¹ The resistances of resistors R_1 and R_2 are selected before starting the measurement of R_x .

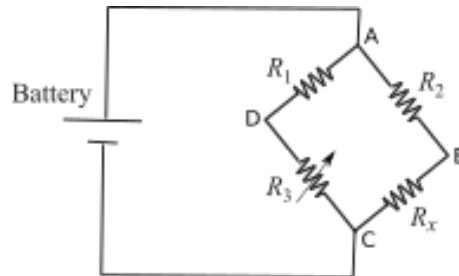


Figure 1. The so-called Wheatstone Bridge. The resistor labeled R_3 is a variable resistor, called a *rheostat*. R_x is some object of unknown resistance that we want to measure by this setup.

The Wheatstone Bridge is both clever and simple. We need only very little theory to understand it, that being Ohm’s Law. Let P and Q be any two distinct points in an electronic circuit. Then the voltage drop between these two points is related to the resistance R and current I between these two points as

$$V = IR. \tag{1}$$

For a Wheatstone Bridge to work, we bridge the gap between points D and B with a galvanometer/ammeter and the adjust the rheostat R_3 until there is no current flowing through it. At this point, certain relationships must be true.

¹I suppose that one could argue that I use Kirchoff’s Law to prove that the current through AD is equal to the current through DC, etc.

First, the current flowing from A to D must be the same as the current flowing from D to C. In other words,

$$I_1 = I_3. \quad (2)$$

By similar reasoning,

$$I_2 = I_x. \quad (3)$$

Second, since there is no current flowing between points D and B, even though they are connected by a conductor, then the potential at D must equal the potential at B. But that implies that the potential difference between points A and D must equal the potential difference between point A and B, or $V_{AD} = V_{AB}$. Thus, by Ohm's Law

$$I_1 R_1 = I_2 R_2. \quad (4)$$

And by similar reasoning,

$$I_3 R_3 = I_x R_x. \quad (5)$$

On dividing (5) by (4), we get

$$\frac{I_3 R_3}{I_1 R_1} = \frac{I_x R_x}{I_2 R_2}. \quad (6)$$

We can now simplify by using (2) and (3):

$$\frac{R_3}{R_1} = \frac{R_x}{R_2}. \quad (7)$$

Solving for R_x , we get the formula we need.

$$R_x = \frac{R_2 R_3}{R_1}. \quad (8)$$